

DEPARTMENT OF COMPUTER SCIENCE & TECHNOLOGY

"T1 Examination, February-2019"

Semester: IV

Subject: COMPUTER ARCHITECTURE & ORGANISATION

Branch: CSE

Course Type: Core

Time: 90 Minutes

Program: B.Tech

Date of Exam: 04/02/19

Subject Code: CSH210-T

Session: II

Course Nature: Hard

Max.Marks:30

Signature: HOD/Associate HOD: *Hany*

Note: Part A: All questions are compulsory. Each Question carries 2 marks.

Part B: Attempt any two questions. Each Question carries 10 marks.

PART-A

- Q1. (a) Explain Binary representation of integers in Computer? (2)
 (b) What are Performance Metrics? (2)
 (c) State and prove De-Morgan's Law? (2)
 (d) Difference between D Flip flop & T Flip flop? (2)
 (e) Simplify the following Boolean postulate $E = (a' + b') \cdot (a' + b) \cdot (a + b')$ (2)

PART-B

- Q2. (a) Write a note on Store Program Control Concept? (5)
 (b) Perform the operation: (5)
 $(11 \times 10)_2 - (B2)_{16} + (25.74)_{10}$
 And find out the result in Decimal Number system.
- Q3. (a) Explain Decoders? Construct a 4 x 16 decoder, using two 3 x 8 decoders. (5)
 (b) Explain Multi-level viewpoint of a machine with diagram. (5)
- Q4. (a) Flynn's Classification divides computers in four major groups. Justify the statement. (5)
 (b) Simplify the following Boolean expression: (5)
 $F = \sum m(0, 3, 4, 5, 7) + \Phi(8, 9, 10, 11, 12, 13, 14, 15)$ in canonical SOPs and implement them using basic gates.

IBM-360 IBM-710

Ver Neumann